



University of Asia Pacific
Department of Computer Science and
Engineering

Design and Testing Of VLSI Lab
(CSE 458)

Submitted By

Mazharul Islam Sourav

ID: 22101133

Section: C-2

Semester: 4-2

Submitted To

Rashik Rahman


Lecturer

Department of Computer Science
and Engineering


University of Asia Pacific

Nor

Stick Diagram Design –

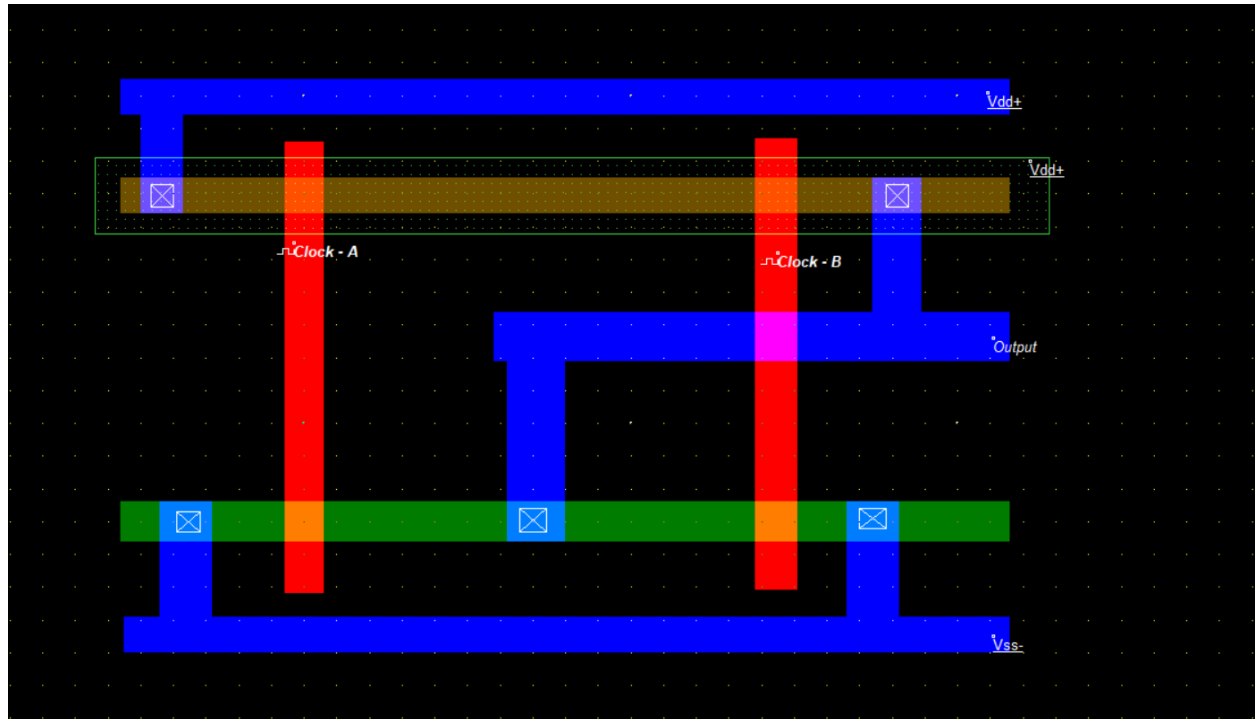


Output –

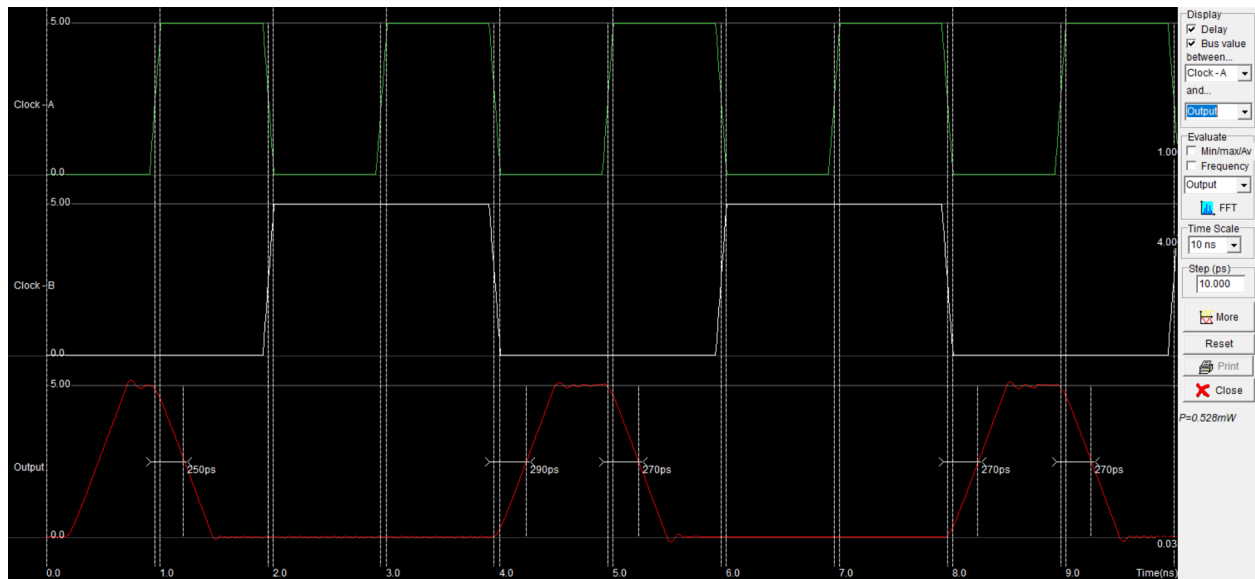

$$A * B * (C + D)$$

Stick Diagram Design –

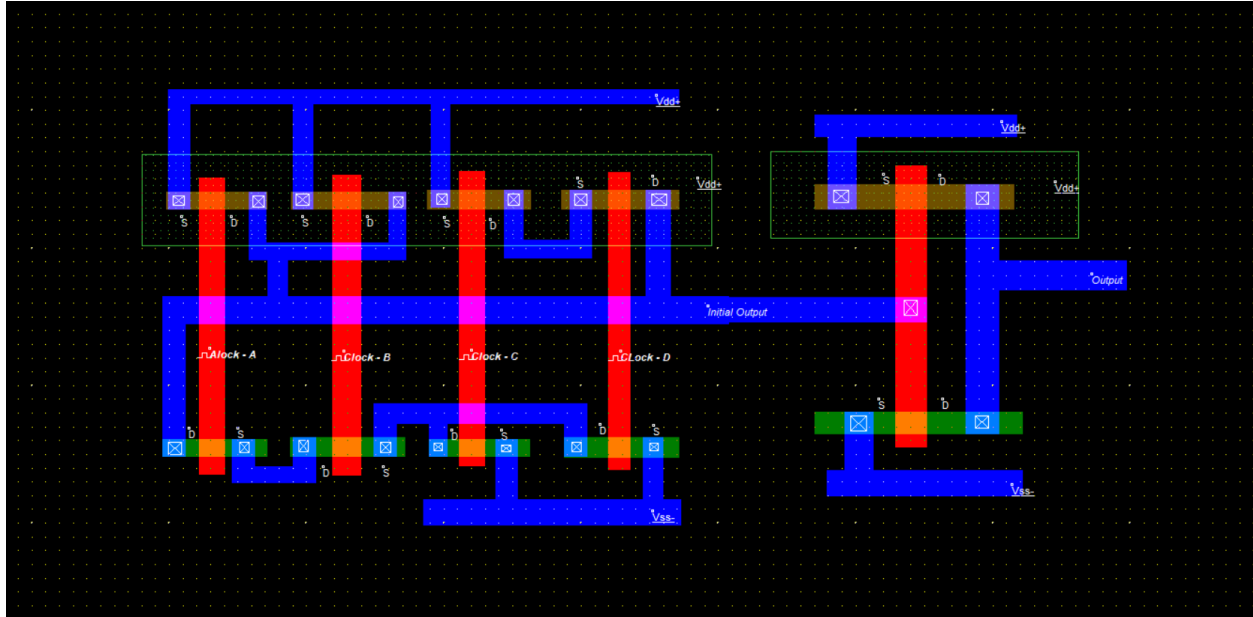

Output –

